

---

## EE273 Lecture 2 Wires

January 12, 2004

Heinz Blennemann  
Stanford University

## Announcements

---

- Please check course webpage regularly for announcements
  - <http://eeclass.stanford.edu/ee273>
- Please register for class

## Today's Assignment

---

- Reading
  - Sections 3.4, 3.6, and 3.7
  - Complete before class on Wednesday 1/16


## Outline

---

- Electrical properties of wires
- Equivalent model of an ideal transmission line
- Derivation of the Telegrapher's equation
- Lossy lines
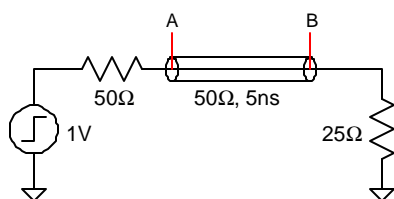
## Last Time

- Three rules of transmission lines
  - Waves propagate down the line (in both directions)
  - Waves reflect unless terminated
  - The voltage on the line is the *superposition* of these waves



$$k_r = \frac{Z_T - Z_0}{Z_T + Z_0} =$$


EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

5
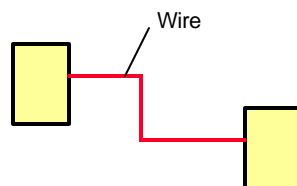
## Wires in Digital Systems

- Physically wires are
  - Microstrip and stripline on printed-circuit cards and backplanes
  - Conductors in cables, cable assemblies
  - Connectors
- We tend to treat them as *ideal wires*
  - no delay (equipotential)
  - no capacitance, inductance, or resistance
- They are *not* ideal
- To build reliable systems we need to understand their properties and behavior




EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

6

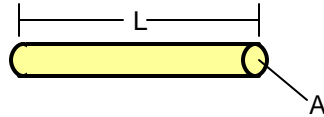
## Resistance of Wires

- Most *real* wires have resistance
- Depends on
  - material (resistivity)
  - length
  - cross section
- Causes
  - delay
  - loss



$$R = \frac{rL}{A}$$

Material	$\rho$ (n $\Omega$ -m)
Ag	16
Cu	17
Au	22
Al	27

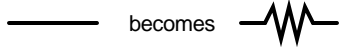


## Capacitance of Wires

- Real wires have capacitance
  - line charge
  - parallel plate
  - fringing
- To compute
  - assume  $Q$
  - compute E field
  - integrate to get  $V$
- Think of the energy stored in the E field


$$C = \frac{Q}{V}$$

$$E = \frac{Q}{2\pi r}$$

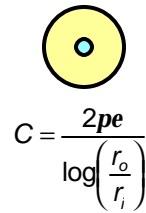


$$C = \frac{2\pi e}{\log\left(\frac{r_o}{r_i}\right)}$$
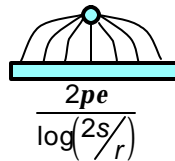
$$C = \frac{2\pi e}{\log\left(\frac{s}{r}\right)}$$


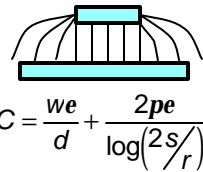
$$\frac{2\pi e}{\log\left(\frac{2s}{r}\right)}$$



$$C = \frac{we}{d} + \frac{2\pi e}{\log\left(\frac{2s}{r}\right)}$$

log is natural logarithm, base e

## Inductance of Wires


- Real wires have inductance

$$L = \frac{\Phi}{I}$$

- In a homogenous medium

$$CL = \epsilon m$$

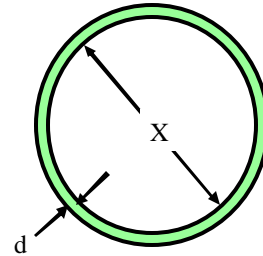- Inductance is a purely geometric property of a **closed** circuit
- Think of the energy stored in the magnetic field



$$L = 3.96 \cdot 10^{-10} X \left( \ln \left[ \frac{8X}{d} \right] - 2 \right)$$

## Some Example Wires

Type	W	R	C	L
On chip	0.6 $\mu$ m	150k $\Omega$ /m	200pf/m	600nH/m
PC Board	150 $\mu$ m	5 $\Omega$ /m	100pf/m	300nH/m
24AWG pair	511 $\mu$ m	0.08 $\Omega$ /m	40pf/m	400nH/m

Scale model of a line has different R, but same L and C per unit length

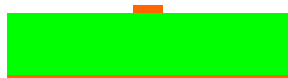
## Qualitative L and C




$$L = L_1, \quad C = C_1, \quad R = R_1$$



$$L = \quad, \quad C = \quad, \quad R = \quad$$


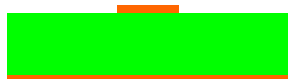
$$L = \quad, \quad C = \quad, \quad R = \quad$$




$$L = \quad, \quad C = \quad, \quad R = \quad$$

## Wire Models


- In a particular situation, we create a *model* of a wire that captures the properties we need
  - ideal
  - lumped L, R, or C
  - RC transmission line
  - LC transmission line
  - General LRCG transmission line
- Model to use depends on frequency

$$f_0 = \frac{R}{2\pi L}$$

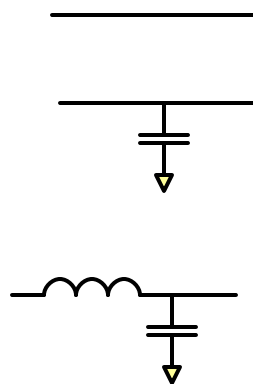

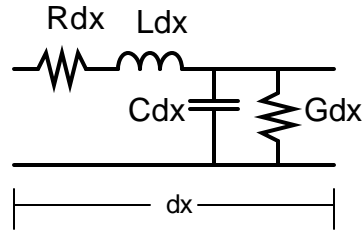
## LRCG Wire Model

- Model an *infinitesimal* length of wire,  $dx$ , with lumped components
  - L, R, C, and G



## Transmission Line Equations

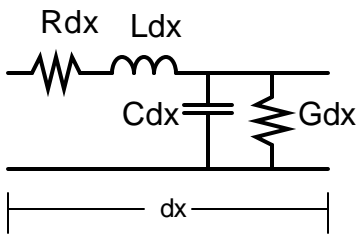

Drop across R and L  $\frac{\partial V}{\partial x} = RI + L \frac{\partial I}{\partial t}$

Current into C and G  $\frac{\partial I}{\partial x} = GV + C \frac{\partial V}{\partial t}$




$$\frac{\partial^2 V}{\partial x^2} = RGV + (RC + LG) \frac{\partial V}{\partial t} + LC \frac{\partial^2 V}{\partial t^2}$$

## Solving this equation gives us two key properties of the line

- Impedance
  - I-V relationship at terminal
- Propagation constant
  - How a signal propagates down the line
    - How fast
    - How much distortion
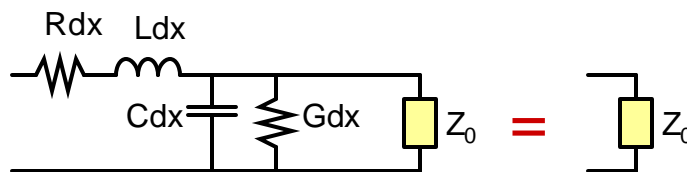
## Impedance

- An infinite length of LRCG transmission line has an *impedance*  $Z_0$
- Driving a line *terminated* into  $Z_0$  is the same as driving  $Z_0$
- In general  $Z_0$  is complex and frequency dependent
- For LC lines its real and independent of frequency



$$Z_0 = \left( \frac{R + Ls}{G + Cs} \right)^{\frac{1}{2}}$$


$$Z_0 = \left( \frac{L}{C} \right)^{\frac{1}{2}}$$

At high frequency (LC lines)
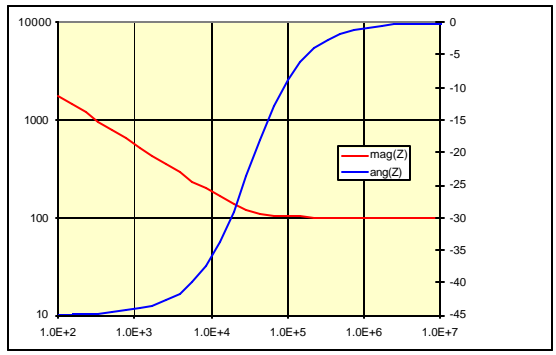
### Example, 24AWG Pair

- $f_0 = 33\text{kHz}$
- Below  $f_0$ , line is RC
- Above  $f_0$ , line is LC


$$Z_0 = \left( \frac{.08 + 400 \times 10^{-9} \times 2\pi f j}{40 \times 10^{-9} \times 2\pi f j} \right)^{\frac{1}{2}}$$


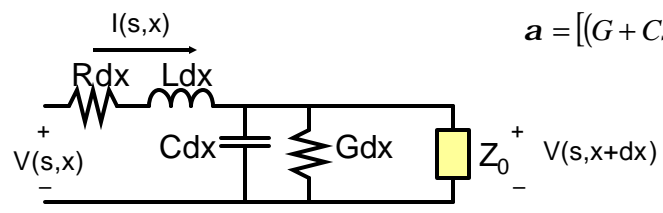
### Propagation Constant

- Using impedance, we can solve for  $V(s,x)$
- Propagation is governed by a constant,  $\alpha$ 
  - real part is attenuation
  - imaginary part is phase shift
    - velocity<sup>-1</sup>
    - $v = (LC)^{-1/2}$

$$\begin{aligned} \frac{\partial V(s)}{\partial x} &= -(R + Ls)I(s) \\ &= -(R + Ls)V(s)/Z_0 \\ &= -[(G + Cs)(R + Ls)]^{\frac{1}{2}}V(s) \\ V(s, x) &= V(s,0) \exp(-ax) \\ &= V(s,0) \exp(-a_{RE}x) \exp(-a_{IM}x) \\ a &= [(G + Cs)(R + Ls)]^{\frac{1}{2}} \end{aligned}$$



## Lossless LC Lines

- If R and G are negligible
  - line is lossless (no dissipation)
  - governed by the *wave equation*
- Waves propagate down the line in both directions without distortion
- Line is described by its **impedance** and **velocity**
- For a general LCRG line we have **impedance** and **propagation constant**

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$V_f(x, t) = V \left( 0, t - \frac{x}{v} \right)$$

$$V_r(x, t) = V \left( x_{\max}, t - \frac{x_{\max} - x}{v} \right)$$

$$v = (LC)^{-\frac{1}{2}}$$



$$Z_0 = \left( \frac{L}{C} \right)^{\frac{1}{2}}$$

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

19

## Driving a Line - Equivalent Circuit

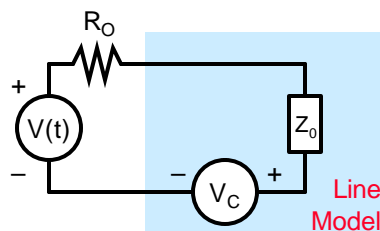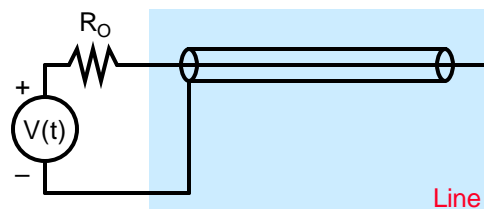


Response of line to voltage source depends on previous state of line,  $V_C$

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

20

## Termination - Equivalent Circuit

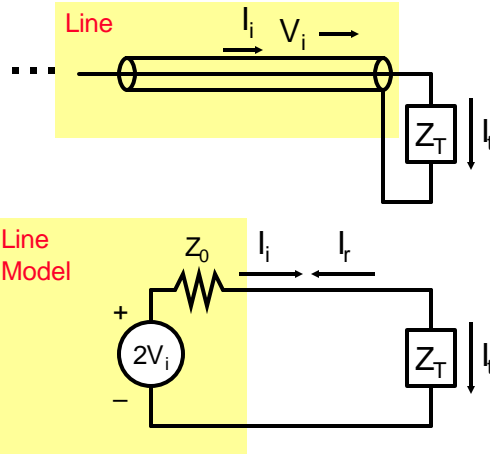

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

21

## Reflections and The Telegrapher's Equation

- Incident wave determines  $V_i, I_i$
- Use equivalent circuit to solve for  $V_r, I_r$
- Use superposition to calculate  $V_r, I_r$


$$I_T = \frac{2V_i}{Z_0 + Z_T}$$

$$I_r = I_i - I_T$$

$$I_r = \frac{V_i}{Z_0} - \frac{2V_i}{Z_0 + Z_T}$$

$$I_r = \frac{V_i}{Z_0} \left( \frac{Z_T - Z_0}{Z_T + Z_0} \right)$$
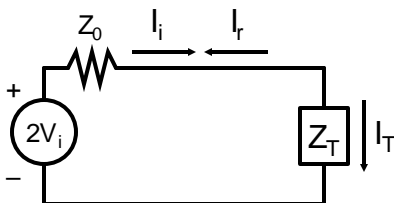
$$\frac{I_r}{I_i} = \frac{V_r}{V_i} = \left( \frac{Z_T - Z_0}{Z_T + Z_0} \right)$$




EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

22
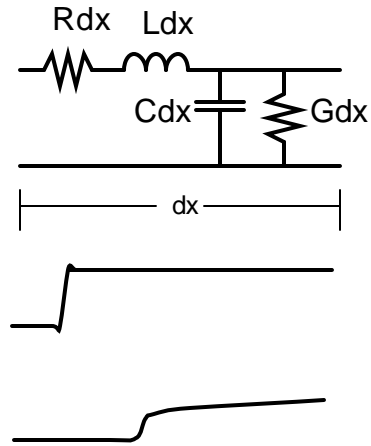
## Lossy Transmission Lines

- LC lines with resistance and conductance
  - propagation mostly by wave
  - some by diffusion
- R and G dissipation
  - reduces the amplitude of the signal
  - disperses the signal
    - fast rise to AC attenuation
    - slow tail to DC attenuation
- Resistance and conductance depend on frequency
  - we will ignore this for now




EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

23

## Zero-th Order Waveform

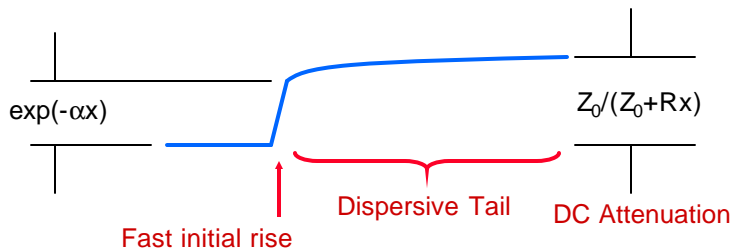

$$a = [(G + Cs)(R + Ls)]^{\frac{1}{2}}$$

EE273, L2





Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

24

Q: So why worry about attenuation?

A: It closes the eye opening!

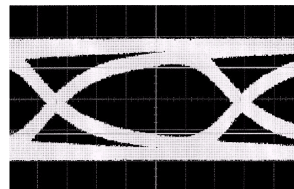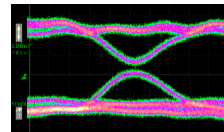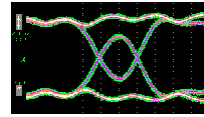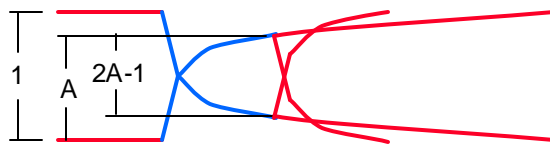- Critical parameter is what fraction of swing,  $A$  is achieved in one bit time
- Eye opening is reduced to  $B = 2A - 1$
- No eye opening at 50% attenuation
- Significant degradation of margins at lower levels of attenuation



EE273, L2


Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

25

## Skin Effect Resistance

- Beauty is only skin deep - so is current
  - current density drops off exponentially with depth
- Skin depth decreases with frequency,  $f^{1/2}$
- Model as if all current flowed in  $\delta$ -thick outer layer of conductor

$$d = (pfms)^{-1/2}$$

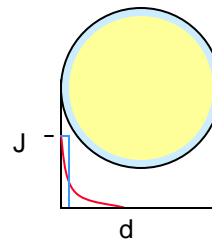

$$J = \exp\left(-\frac{d}{\delta}\right)$$

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

26

## Skin-Effect Resistance

- Effect does not occur until frequency,  $f_s$ , at which skin depth equals conductor radius
- Above  $f_s$ ,  $R$  and  $A$  increase as the square-root of frequency


$$R(f) = \frac{R_{DC}}{2} \left( \frac{f}{f_s} \right)$$

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

27
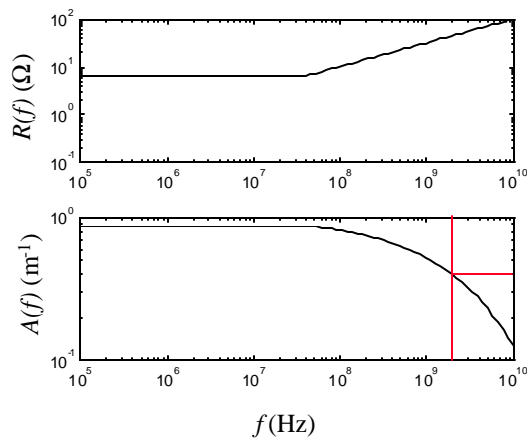
## Resistance and Attenuation of 5mil 0.5oz 50Ω Strippguide



EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

28

## Dielectric Absorption

- High frequency signals *jiggle* molecules in the insulator
  - insulator *absorbs* signal energy
- This effect is approximately linear with frequency and is modeled as a conductance
- Dielectric loss is often specified in terms of a *loss tangent*,  $\tan(\delta)$



$$\tan d = \frac{G}{\omega C}$$

$$a_D = \frac{GZ_0}{2}$$

$$= pf \tan d \sqrt{LC}$$

$$= \frac{p\sqrt{\epsilon_r} f \tan d}{c}$$


material	$\tan \delta$
FR4	0.035
Polyimide	0.025
GETEK	0.010
Teflon	0.001

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

29
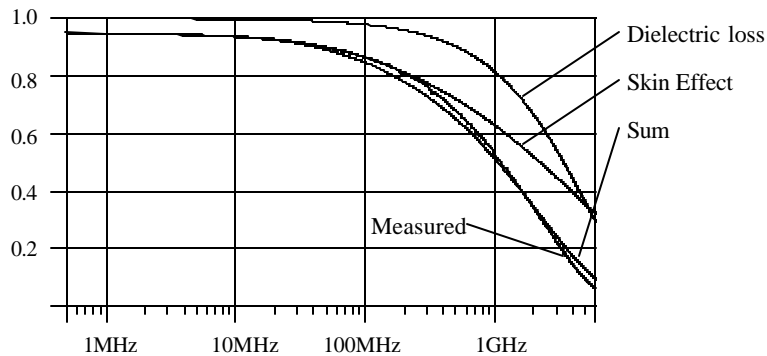
## Skin effect resistance and dielectric absorption



1m 8mil 50Ω stripguide with GETEK dielectric

EE273, L2

Copyright 2004 (c) by WJD &amp; HCB, all rights reserved

30

## The $Bd^2$ Constant

- Suppose you can tolerate a certain attenuation,  $A_1$ 
  - eye opening is  $2A-1$
- At a certain bandwidth,  $B_1$ , attenuation  $A$  is achieved with a distance of 1m
- As bandwidth is increased, resistance, and hence attenuation, increases as  $B^{1/2}$
- So distance must be decreased by a proportional amount

$$A(B_1) = A_1$$

$$A(B, d) = A_1 d \left( \frac{B}{B_1} \right)^{1/2}$$

$$Bd^2 = B_1$$

Doubling distance cuts bandwidth by a factor of 4



## Next Time

- Transmission line wrapup
- Differential lines
- Multi-drop buses