
EE273 Lecture 3

Wires Reviewed

Multidrop Buses, Balanced Lines, and Measurement Techniques

January 14, 2004

Heinz Blennemann
Stanford University

Announcement

- No class or office hours on Monday 1/19 – Stanford Holiday.

Today's Assignment


- Reading
 - Sections 6.1 through 6.3
 - Complete before class on Wednesday 1/21
- Problem set 2
 - see Web page
 - Due at start of class on Wednesday 1/21

A Quick Overview

- Lossy LC Lines
 - Waveform
 - Skin effect and dielectric absorption
- Multi-Drop Buses
 - stubs and discontinuities
 - frequency limitations
- Balanced lines
 - common and differential mode excitation
 - odd and even mode impedance
 - rise on signal is accompanied by fall on return
- Modeling wires
 - build a model to capture relevant electrical properties
 - ignore inessential elements
 - depends on rise time
- Time-Domain Reflectometer
 - oscilloscope plus pulse generator
 - how to interpret the results
 - a demo

Lossy Transmission Lines

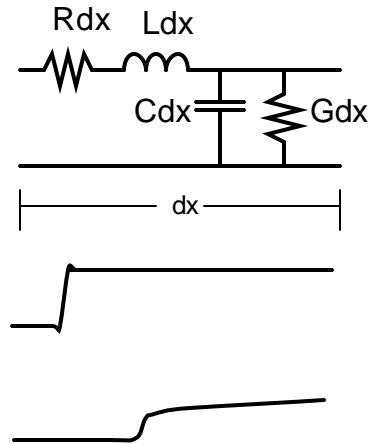- LC lines with resistance and conductance
 - propagation mostly by wave
 - some by diffusion
- R and G dissipation
 - reduces the amplitude of the signal
 - disperses the signal
 - fast rise to AC attenuation
 - slow tail to DC attenuation
- Resistance and conductance depend on frequency
 - we will ignore this for now




EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

5

Zero-th Order Waveform

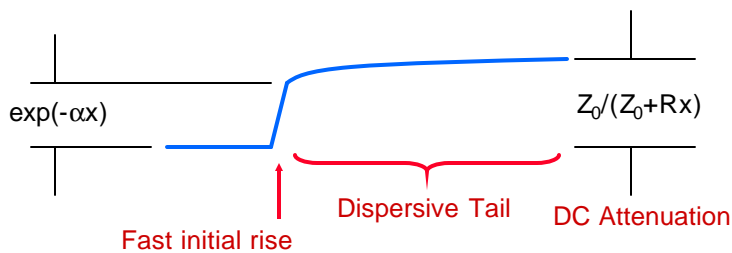


$$a = [(G + Cs)(R + Ls)]^{\frac{1}{2}}$$

EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved


6

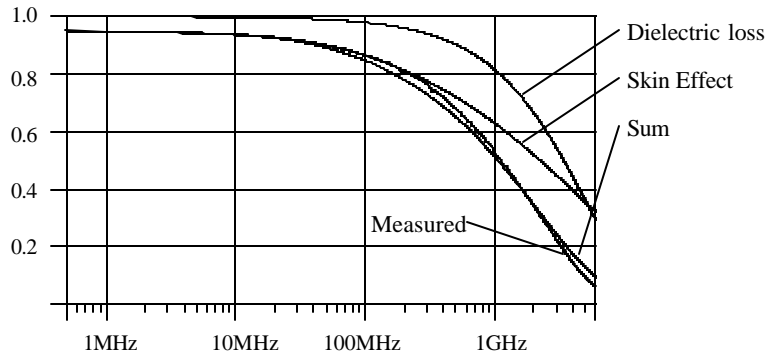Skin effect resistance and dielectric absorption



1m 8mil 50Ω stripguide with GETEK dielectric

Multi-drop Buses


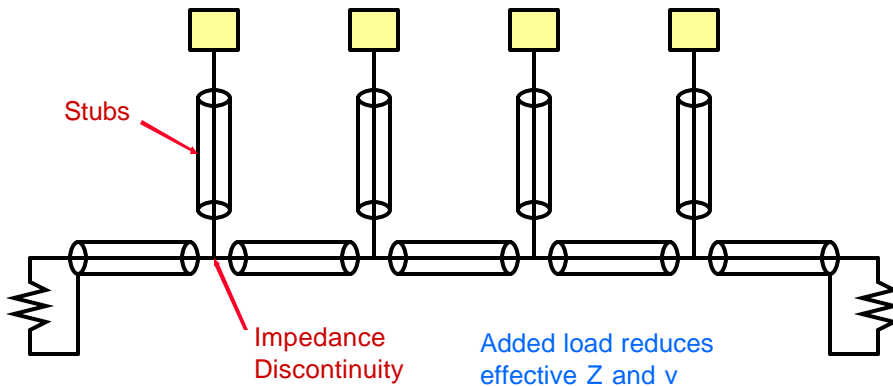


Multi-Drop Buses



- Consider a typical bus
 - 50Ω PC board traces
 - $C = 100\text{pF/m}$, $L=300\text{nH/m}$
 - Stubs are 10cm long (0.7ns)
 - 20pF load at end
 - Spacing between modules is 3cm
- Constraints:
 - rise time must be *long* compared to stub length (>3ns) and spacing (>1ns)
 - 30pF each 3cm brings C to 1100pF/m
 - $Z = 16.5\Omega$, $v=5.5 \times 10^7$ m/s
 - driver sees 8.25Ω
- Bus speed is limited by geometry of the bus
 - stub length
 - stub spacing
- Leaving a module 'unplugged' causes a discontinuity
- Point-to-point signaling
 - is electrically much cleaner
 - allows concurrent transfers
- 'Just say no' to buses
- If you must use a bus, 'fold' the stubs

Balanced Transmission Lines

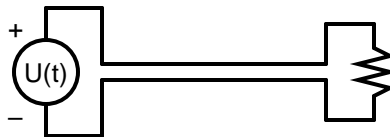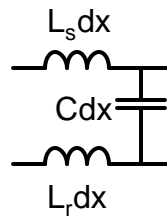- All transmission lines have inductance in the return path
 - leads to a shift in return voltage across line
- In a balanced line, return inductance equals signal inductance
- Suppose we put a 1V step into a balanced line
 - 0.5V drop across signal inductor
 - 0.5V drop across return inductor
- Remember, we can only name one point GND





Even and Odd Mode Impedance

 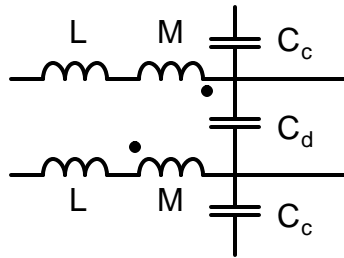

e.g., pair of strip guides
between ground planes


- M and C_d represent coupling between lines
- L and C_c represent coupling to other conductors

Common and Differential Mode Excitation

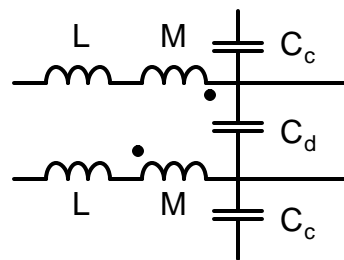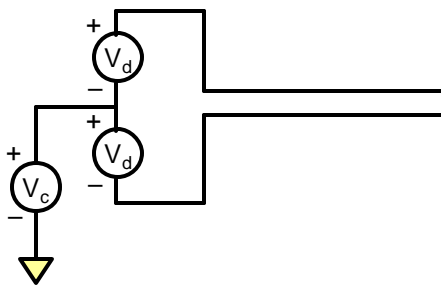

- Any excitation can be described as the superposition of a *differential signal* and a *common-mode signal*
- e.g. 1V step: $V_c = 0.5V$, $V_d = 0.5V$

Even and Odd Mode Impedance

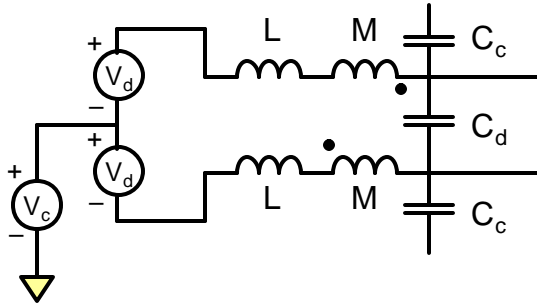

$$Z_O = \frac{V_D}{I_1} = \left(\frac{L-M}{C+C_D} \right)^{1/2}$$

$$Z_E = \frac{V_C}{I_1} = \left(\frac{L+M}{C-C_D} \right)^{1/2}$$

$$C = C_C + C_D$$


$$\frac{L}{M} = \frac{C}{C_D}$$

- Common and differential-mode signals see different impedance

Definitions


- Even-mode impedance, Z_E
 - impedance seen on each line by a common-mode signal
- Odd-mode impedance, Z_O
 - impedance seen on each line by differential mode signal
- Differential impedance, $Z_D = 2Z_O$
 - impedance seen across a pair of lines by differential mode signal
- Common-mode impedance, $Z_C = 0.5Z_E$
 - impedance seen between a pair of lines and a common return by a common-mode signal.

Example of Even and Odd mode impedances

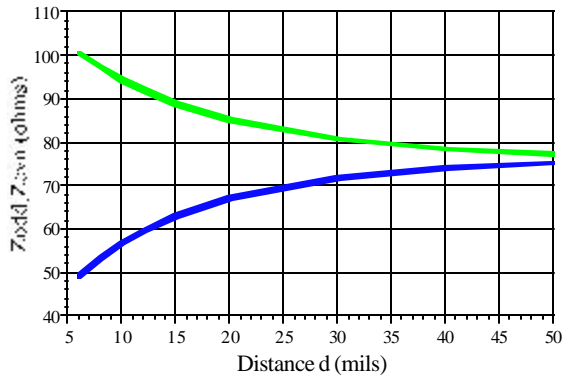


22 8 d 22

Terminating Even and Odd Modes

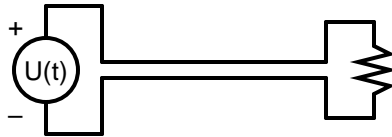

- Suppose $Z_O=50\Omega$ and $Z_E=100\Omega$.
- What happens to a 1V step on the line above?
- How should the line be terminated?
- Mode coupling

Terminating Even and Odd Modes

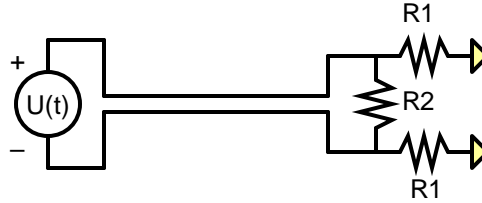

$$R1 = Z_E$$


$$R2 = 2 \left(\frac{Z_E Z_O}{Z_E - Z_O} \right)$$

$$Z_O = R1 \parallel R2$$





Modeling of Wires

- Given a real system
 - chips, packages, boards, connectors, backplanes, cables
- Need to develop a *model* of the signaling medium
 - for hand calculation of key properties
 - for SPICE simulations
- Model must
 - capture all *relevant* wire properties
 - transmission line properties
 - major discontinuities
 - terminations
 - ignore those that are not relevant
 - e.g., short discontinuities
- A good model captures the *relevant* behavior while being as simple as possible

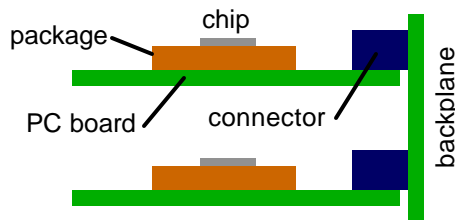

Example Model

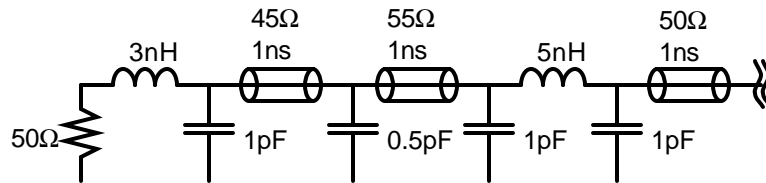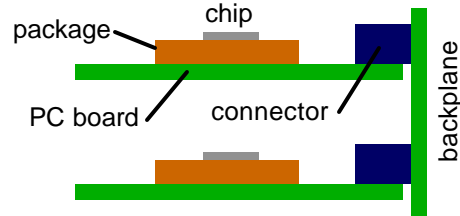


EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

19

Deriving a Model

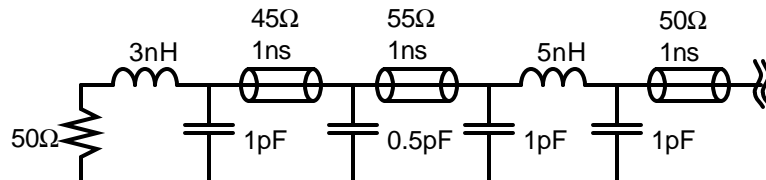- How do we make a model of a signal path?
 - hand calculation
 - assemble models from component, connector, and package vendors
 - CAD programs
 - measurements of the actual system




EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

20

Meet the Time-Domain Reflectometer

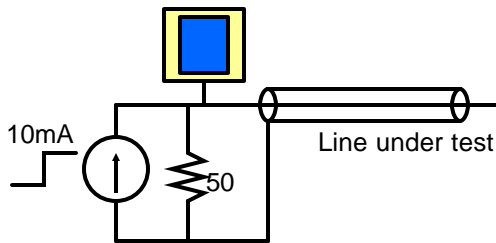- A time-domain reflectometer is a fast step generator and a high-speed oscilloscope.
- To characterize a line
 - inject a fast (usually 20ps) step into the line
 - observe the reflected waveform
 - what does it mean?



EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

21

The Sampling Scope/ Time-Domain Reflectometer

- HP 54750A Sampling Scope
 - 54754A Differential TDR head
 - 45ps step generator
 - dual 18GHz sampling heads
 - 54751A Sampling head
 - dual 20GHz samplers
 - inputs +/- 2V Max!
 - 3.5mm/SMA connectors




EE273, L3, Jan 14, 2004


Copyright 2004 (C) by WJD & HCB, All Rights Reserved

22


TDR of Basic Line

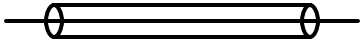


Open circuit



Matched termination

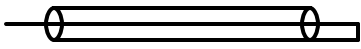


Short circuit

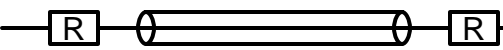

Unterminated

EE273, L3, Jan 14, 2004
Copyright 2004 (C) by WJD & HCB, All Rights Reserved
23

Open Line

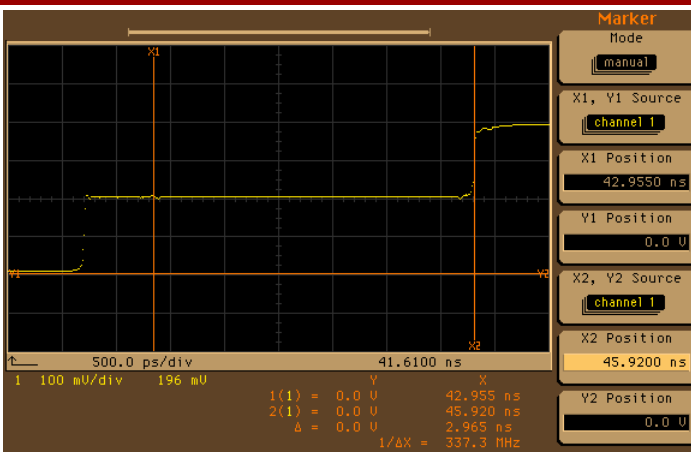


3.0 ns from start of line to reflection implies line is ____ ns long


EE273, L3, Jan 14, 2004
Copyright 2004 (C) by WJD & HCB, All Rights Reserved
24

Open Line

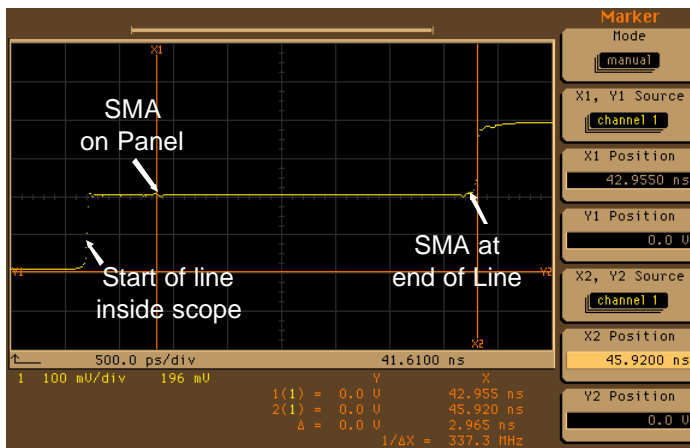Compare slope of edge at start of line with slope after two round trips.



Matched Termination

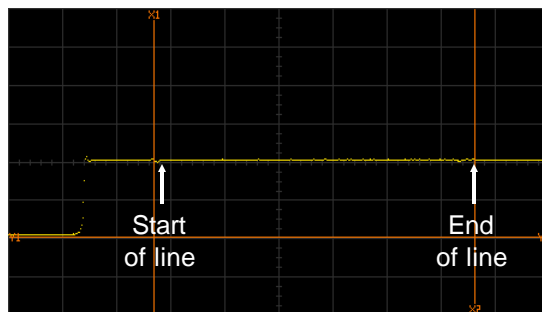

Short Circuit




EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

27

“Ring-Up” of Underterminated Line

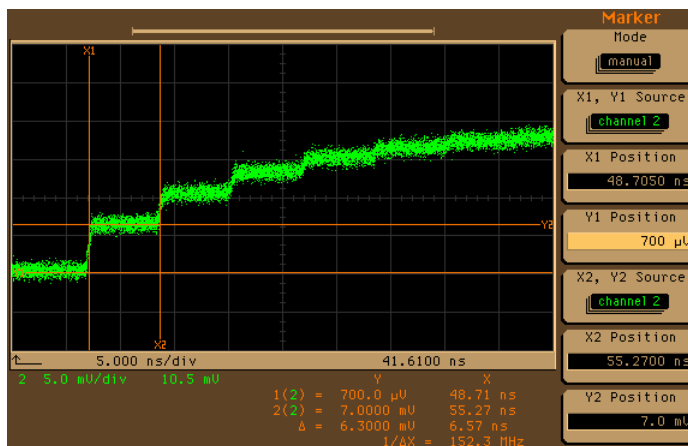


EE273, L3, Jan 14, 2004


Copyright 2004 (C) by WJD & HCB, All Rights Reserved

28

Close-up of TDR Rise-Time

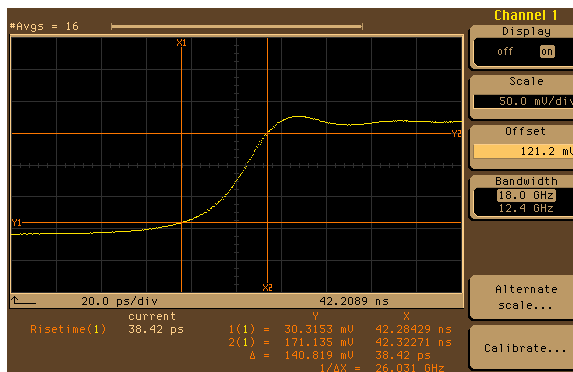

What made these waveforms?

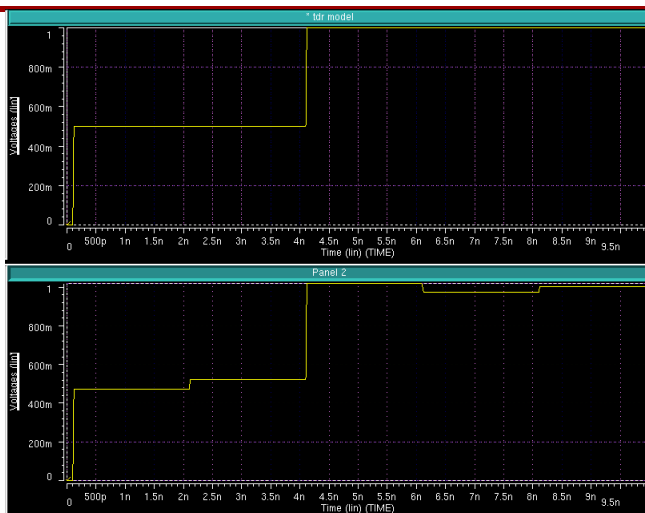


Calculating Impedance from Voltage

$$V = \frac{Z}{Z + Z_0}$$

$$(Z + Z_0)V = Z$$
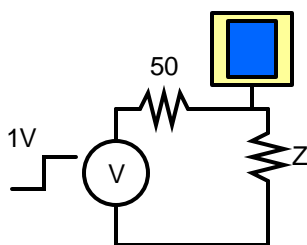
$$Z = Z_0 \left(\frac{V}{1 - V} \right)$$



V	Z
0.50	50.0
0.47	44.3
0.53	56.4



EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

31

Time of Observation is Round Trip
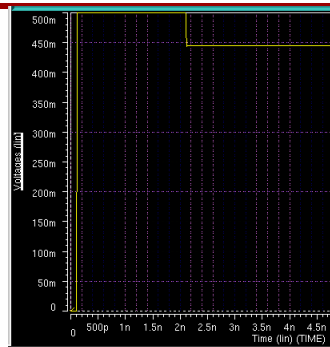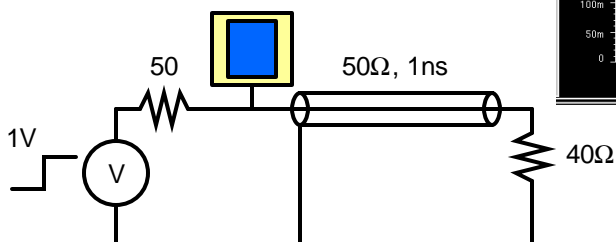
$$Z(x) = Z_0 \left(\frac{V(2x/v)}{1 - V(2x/v)} \right)$$




EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved


32

What About Inductors and Capacitors?

$$L = 2Z_0 t_L$$

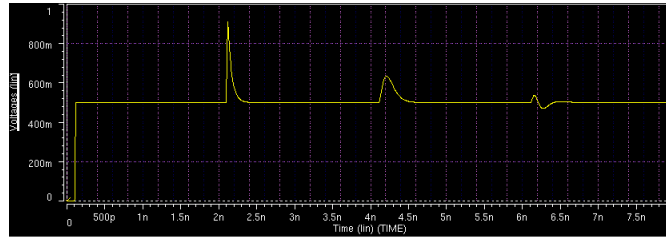

$$C = \frac{2t_C}{Z_0}$$

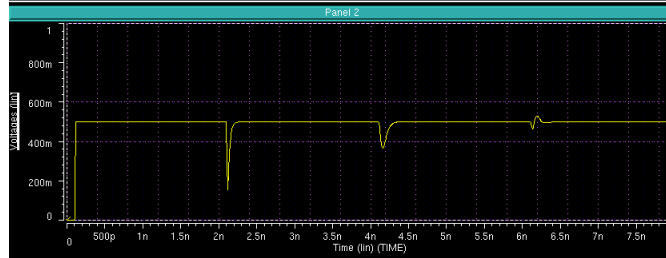

EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

33

Rise-Time Degradation

- Upstream elements (Ls & Cs) low-pass the signal resulting in a longer rise-time
- This affects the reflections from down-stream elements
 - slow rising edge
 - spread out response (convolution with slow edge)
 - L & C responses don't go full swing
- This makes it
 - hard to extract exact L and C values
 - impossible to measure very small discontinuities
 - but if the TDR can't see them, neither can the signal

EE273, L3, Jan 14, 2004


Copyright 2004 (C) by WJD & HCB, All Rights Reserved

34


Extraction Procedure

- Identify regions of the TDR plot as
 - flat region - transmission line
 - bump up - inductor
 - bump down - capacitor
- Starting at source
 - determine value of Z & t , L , or C for nearest element
 - simulate to validate and determine new t_r
 - iterate as needed to get value right
 - move on to next element
- Don't need model with more resolution than your fastest rise time

Example TDR Trace

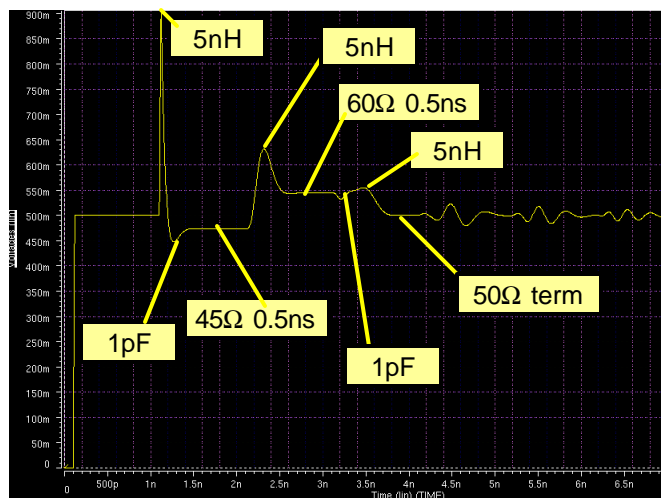

Same waveform with 200ps edge

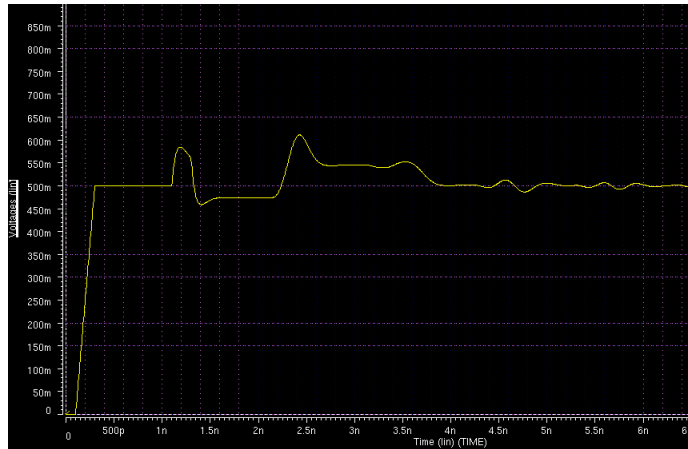

EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

37

Next Time

- Noise
 - what disturbs digital signals
 - fixed and proportional noise
- Power Supply Noise
 - single supply and differential
 - sources
- Cross Talk
 - capacitive crosstalk
 - transmission lines

EE273, L3, Jan 14, 2004

Copyright 2004 (C) by WJD & HCB, All Rights Reserved

38